

Final Project Report:

Elevator Control Unit

Brandon Bernier & Christopher Graham

ECE 4140: VLSI Design and Simulation

Professor Proie

December 3, 2013

1. Introduction

The proposed project is an elevator control unit. The system will control three elevators that have the ability to travel up and down to a maximum of seven floors. The theory of operation is very similar to how real elevators work. There will be both call buttons at each floor as well as buttons inside the elevator. When a floor has been selected, an elevator will go up or down to that floor. The elevator that is closest to the floor call that has been selected will be the one that responds. The elevator system makes use of both combinational and sequential logic to make decisions and operate as desired. This project is a great example of a finite state machine that must make decisions based on the current state or position of all three elevators.

2. Overall System Design

The system will specifically allow three elevators to operate independently across seven floors in order to serve requests as efficiently as possible. Initially it was intended to have the system serve eight floors, however, 000 was not a viable input because there was no way to distinguish it from no input. Therefore, the design had to be limited to seven floors of operation. Originally, it was also desired to have the control unit keep track of multiple button presses, and sequentially progress through them. This functionality was found to require a lot of extra logic that would have ballooned the overall transistor count to a range that was felt could not fit in the given bounds of the chip. This was simplified, and the system can currently only handle a single request at a time for the buttons inside each elevator. The inputs are received by the control unit, stored, and then used to compute the best path of each of the elevators. Logic within the system will assist with determining the most efficient path for all three elevators. The system then communicates with each elevator car by outputting a 3-bit number representing the floor that the elevator must progress to.

The system is initialized with all three elevators in a 0 state, meaning the register holding its current location starts at 0. Each elevator must be called at least once to leave this output state and give an actual floor for where the elevator should be located. Technically, any elevator in the 0 state would be sitting at the 1st floor, but it will only output that once it is called to move somewhere. After this, it never again returns to the 0 state.

Another important design decision was the decision to copy and paste layouts into bigger modules instead of simply instantiating them. This allowed for a lot of flexibility when hand routing because the lower-level gates were not always designed perfectly for inclusion in the bigger project. This also allowed us to change the size of the V_{DD} and GND rails to 3 contacts wide and expand all the way down a row of components. A thick V_{DD} and GND rail ensures that they can source enough current to all of the components connected to them without any trouble. This decision made it very easy to connect multiple sub-blocks into bigger modules as well as the final overall layout. It was very simply to connect the rails with large strips of metal out to the pads.

Inputs and Outputs

There are 25 input and outputs for this design, excluding power, ground, and the clock. This is further broken down to 16 inputs and 9 outputs. The inputs will consist of the buttons at each floor to call the elevator and the individual floor buttons inside the elevator. The decision to design this system for 3 elevators in a building of up to 7 floors was directly related to the number of I/O pins that would be available. Each floor has a single button with which an elevator can be called. Within each elevator, there will be 7 buttons to get to each of the seven floors. This totals 21 buttons across all three elevators. The system will assume that these buttons are externally encoded to a 3-bit number. That allows us to reduce the necessary inputs from these buttons from 21 to only 9. The control unit will then have 9 output pins, 3 going to each elevator. These outputs will represent the floor that the elevator must travel to. The 3-bit number will be decoded externally to signify floors 1 through 8. This output would be fed to another system powering the actual elevator motors and is simply telling that separate module where to move each elevator.

 


Figure 1: Context Diagram of the Elevator Control Unit Showing Inputs & Outputs

 


Figure 2: Top-Level Schematic of the Entire System

Area/Floor Plan

An original estimation for the total number of transistors necessary for the design brought us to between 3,000 and 3,500 transistors total. The actual final transistor count was 3764. From this rough estimation, we predicted that the design would require anywhere between 0.75mm² and the full 0.9mm² of usable area. The final dimensions of the system layout are roughly 780x760µm, for a total area of only 0.593mm². The final area came in much smaller than expected for this number of transistors due to a lot of work on the layouts ensuring they were as compact and efficient as possible. Even in the final design, there is a noticeable amount of blank space between many of the modules, which could have easily been avoided to condense the design down even further. The exact floor plan of the final modules within the PAD frame follows below.

 


Figure 3: Accurate Layout Floor Plan Showing Major Modules

Group Breakdown


The breakdown of work for this project is as follows. Brandon focused on the necessary memory elements in the design including all of the data registers. He also verified the layout and operation of all of the simple gates and blocks necessary for the design. Brandon was also tasked with testing the system. Together we designed the necessary components for the overall schematic of the system. Brandon debugged the schematic to the point where we were able to have all three elevators functioning as expected. Brandon also handled the majority of the layout for the system including the major modules as well as the final overall layout, PAD frame placement, and GDS tape out. Chris focused on completion of the schematic and verification of each sub-block. He was responsible for compiling the majority of the figures and verification results of the individual modules for the final report.

3. Lower-Level Design Implementation


Full Adder

A one-bit full adder adds two one-bit numbers A and B. The full adder is used to create a 3-Bit full adder.

Inputs	Outputs
A	S
B	Cout
Cin	

 


Full Adder Schematic

 

Full Adder Symbol



 Full Adder Layout (Area $\approx 25 \times 90 \mu\text{m}$)



Full Adder Extracted View

```
@(#) $CDS: LVS version 6.1.5 05/04/2012 23:29 (sjfdl224) $
```

```
Command line: /apps/cadence/ic6155/tools.lnx86/dfII/bin/32bit/LVS -dir /home/seas/c
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...
```

```
Net-list summary for /home/seas/crgraham/cadence/LVS/layout/netlist
```

```
count
26      nets
7       terminals
21      pmos
21      rmos
```

```
Net-list summary for /home/seas/crgraham/cadence/LVS/schematic/netlist
```

```
count
26      nets
7       terminals
21      pmos
21      rmos
```

```
Terminal correspondence points
```

```
N22      N6      A
N21      N7      B
N24      N9      Cin
N25      N5      Cout
N20      N2      S
N19      N0      gnd!
N23      N1      vdd!
```

```
Devices in the netlist but not in the rules:
```


```
pcapacitor
```

```
Devices in the rules but not in the netlist:
```

```
cap nfet pfet rmos4 pmos4
```

```
The net-lists match.
```

Full Adder LVS Report

 


Full Adder Simulation


3-Bit Full Adder

The three bit full adder adds two three bit binary numbers. The three bit full adder is made from three full adders. The three bit full adder is used in the elevator control unit to do the addition in the adder subtractor module.


Inputs	Outputs
A0	S0
B0	S1
A1	S2
B1	Cout
A2	
B2	
Cin	

 


3-Bit Full Adder Schematic

 


3-Bit Full Adder Symbol

 

 
3-Bit Full Adder Layout (Area $\approx 109 \times 102 \mu\text{m}$)



3-Bit Full Adder Extracted View

 

3-Bit Full Adder LVS Report

 


3-Bit Full Adder Simulation


2-to-1 MUX

A multiplexer selects either input A or B to be outputted. The multiplexer is used to create a 4 to 1 multiplexer.



Inputs	Outputs
A	OUT
B	
S	

 

2-to-1 MUX Schematic

 

2-to-1 MUX Symbol

  

```

@(#)SCDS: LVS version 5.1.5 05/04/2012 23:29 (sjfd1234) 3
Command line: /apps/cadence/ic6155/tools.lvs86/dft11/bin/32bit/LVS -dir /home/seas/i
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Drive LVS rules...

Net-list summary for /home/seas/crgraham/cadence/LVS/Layout/netlist
count
7      nets
6      terminals
3      pins
3      pins

Net-list summary for /home/seas/crgraham/cadence/LVS/schematic/netlist
count
7      nets
6      terminals
3      pins
3      pins

Terminal correspondence points
N5      N2      A
N4      N0      B
N3      N5      OUT
N2      N4      S
N1      N0      gnd!
N6      N1      vdd!


Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nfet pfet rmos4 pmos4

The net-lists match.

          layout schematic
          instances
un-matched      0      0
revired         0      0
size errors     0      0
pruned         0      0
active          6      6
total          6      6

```

2-to-1 MUX LVS Report

 


2-to-1 MUX Simulation


4-to-1 MUX

The 4 to 1 multiplexer consists of three 2 to 1 multiplexers. The 4 to 1 multiplexer operates the same way as a 2 to 1 multiplexer but has more inputs. The 4 to 1 multiplexer is used in the elevator control unit to create the 3 bit adder subtractor module.


Inputs	Outputs
A	OUT
B	
C	
D	
S0	
S1	

 


4-to-1 MUX Schematic

 

4-to-1 MUX Symbol

 

 4-to-1 MUX Layout (Area $\approx 31.8 \times 39 \mu\text{m}$)



4-to-1 MUX Extracted View

```

@(#)SCDS: LVS version 6.1.5 05/04/2012 23:29 (sjfd1224) $

Command line: /apps/cadence/ic6155/tools.lnx86/dfII/bin/32bit/LVS -dir /home/sea
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...

Net-list summary for /home/sea/crgraham/cadence/LVS/layout/netlist
count
14      nets
9       terminals
9       pmos
9       rmos

Net-list summary for /home/sea/crgraham/cadence/LVS/schematic/netlist
count
14      nets
9       terminals
9       pmos
9       rmos


Terminal correspondence points
N12     N6      A
N11     N2      B
N10     N8      C
N9      N3      D
N8      N5      OUT
N6      N4      S0
N5      N10     S1
N7      N0      gnd!
N13     N1      vdd!

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nfet pfet rmos4 pmos4

The net-lists match.

```

4-to-1 MUX LVS Report

 


4-to-1 MUX Simulation


3-Bit Adder Subtractor

The 3 bit adder subtractor consists of 4 to 1 multiplexers, 3 bit adders, and xor gates. The 3 bit adder subtractor either subtracts or adds two three bit numbers depending on the input. The 3 bit adder subtractor is used in the comparison module to figure out which elevator is closest to the floor selected.


Inputs	Outputs
A0	S0
B0	S1
A1	S2
B1	
A2	
B2	
Sub	

 


3-Bit Adder Subtractor Schematic

 

3-Bit Adder Subtractor Symbol

 

 3-Bit Adder Subtractor Layout (Area $\approx 149 \times 209 \mu\text{m}$)



3-Bit Adder Subtractor Extracted View

```
@(#)SCDS: LVS version 6.1.5 05/04/2012 23:29 (sjfd1224) $
Command line: /apps/cadence/ic6155/tools.lnx86/dfII/bin/32bit/LVS -dir /home/seas/crgraham/cadence/LVS/layout/netlist
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...

Net-list summary for /home/seas/crgraham/cadence/LVS/layout/netlist
count
193      nets
12       terminals
189      pmos
189      rmos


Net-list summary for /home/seas/crgraham/cadence/LVS/schematic/netlist
count
193      nets
12       terminals
189      pmos
189      rmos

Terminal correspondence points
N186      N24      A0
N185      N16      A1
N184      N4       A2
N192      N9       B0
N191      N28      B1
N190      N14      B2
N183      N13      S0
N182      N29      S1
N181      N25      S2
N189      N2       Sub
N187      N0       gnd!
N188      N1       vdd!

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nfet pfet rmos4 pmos4

The net-lists match.
```

3-Bit Adder Subtractor LVS Report

 


3-Bit Adder Subtractor Simulation


D Flip Flop

The d flip flop is used to create memory in the elevator control unit. A single d flip flop will store a data value for a clock cycle. D flip flops are cascaded together to create registers.


Inputs	Outputs
D	Q
CLK	Q_bar
CLRn	

 


D Flip Flop Schematic

 

D Flip Flop Symbol

 

 D Flip Flop Layout (Area $\approx 31.8 \times 58 \mu\text{m}$)



D Flip Flop Extracted View

@(#)\$CDS: LVS version 6.1.5 05/04/2012 23:29 (SJ101224) \$

Command line: /apps/cadence/ic6155/tools.lnx86/dfII/bin/32bit/LVS -dir /home/s
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...

Net-list summary for /home/seas/crgraham/cadence/LVS/layout/netlist

count	
21	nets
7	terminals
16	pmos
16	nmos

Net-list summary for /home/seas/crgraham/cadence/LVS/schematic/netlist

count	
21	nets
7	terminals
16	pmos
16	nmos

Terminal correspondence points


N18	N8	CLK
N15	N3	CLRn
N19	N9	D
N16	N4	Q
N17	N10	Q_bar
N14	N0	gnd!
N20	N1	vdd!

Devices in the netlist but not in the rules:
pcapacitor

Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4

The net-lists match.


D Flip Flop LVS Report

 


3-Bit Register

The 3 bit register consists of three d flip flops. The register stores three data values every clock cycle. The register is used in the elevator control unit to store the values of button presses.


Inputs	Outputs
D0	Out0
D1	Out1
D2	Out2
CLK	
CLRn	

 


3-Bit Register Schematic

 

3-Bit Register Symbol

 

 3-Bit Register Layout (Area $\approx 108 \times 65 \mu\text{m}$)



3-Bit Register Extracted View

```

@(#) $CDS: LVS version 6.1.5 05/04/2012 23:29 (sjfd1224) $

Command line: /apps/cadence/ic6155/tools.lnx86/dfII/bin/32bit/LVS -dir /home/
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...

Net-list summary for /home/seas/crgraham/cadence/LVS/layout/netlist
count
55      nets
10      terminals
48      pmos
48      rmos

Net-list summary for /home/seas/crgraham/cadence/LVS/schematic/netlist
count
55      nets
10      terminals
48      pmos
48      rmos


Terminal correspondence points
N50      N7      CLK
N47      N10     CLRn
N54      N4      D0
N53      N12     D1
N52      N11     D2
N49      N8      Out0
N48      N9      Out1
N46      N3      Out2
N45      N0      gnd!
N51      N1      vdd!

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nfet pfet rmos4 pmos4

The net-lists match.

```

3-Bit Register LVS Report

 


3-Bit Register Simulation


8-Bit Register

The 8 bit register is similar to the 3 bit register in terms of operation. The 8 bit register stores eight data inputs every clock cycle. The 8 bit adder is used to store the locations of each elevator.


Inputs	Outputs
D0	Q0
D1	Q1
D2	Q2
D3	Q3
D4	Q4
D5	Q5
D6	Q6
D7	Q7
CLK	
CLRn	

 


8-Bit Register Schematic

 

8-Bit Register Symbol

 

8-Bit Register Layout (Area ≈ 143x125μm)

 

8-Bit Register Extracted View

```
Net-list summary for /home/seas/crgraham/cadence/LVS/layout/netlist
count
140      nets
20       terminals
128      pmos
128      rmos
```

```
Net-list summary for /home/seas/crgraham/cadence/LVS/schematic/netlist
count
140      nets
20       terminals
128      pmos
128      rmos
```

```
Terminal correspondence points
N130     N16      CLK
N129     N27      CLRN
N139     N19      D0
N138     N25      D1
N137     N13      D2
N136     N23      D3
N135     N22      D4
N134     N26      D5
N133     N9       D6
N132     N7       D7
N128     N24      Q0
N127     N10      Q1
N126     N18      Q2
N125     N17      Q3
N124     N20      Q4
N123     N15      Q5
N122     N12      Q6
N121     N8       Q7
N120     N0       gnd!
N131     N1       vdd!
```

Devices in the netlist but not in the rules:

pcapacitor

Devices in the rules but not in the netlist:

cap nfet pfet rmos4 pmos4


The net-lists match.

8-Bit Register LVS Report


3-Bit Comparator

The 3 bit comparator is used to compare two binary numbers. The 3 bit comparator is used in the comparison module to compare the location of each elevator.


Inputs	Outputs
A0	AltB
B0	AgB
A1	AeqB
B1	
A2	
B2	

 


3-Bit Comparator Schematic

 

3-Bit Comparator Symbol

 

 3-Bit Comparator Layout (Area $\approx 110 \times 73 \mu\text{m}$)




3-Bit Comparator Extracted View


8-to-3 Encoder

The 8 to 3 encoder converts multiple inputs into a binary signal. The 8 to 3 encoder is used in the floor call module to encode the floor button presses into a binary number.


Inputs	Outputs
IN0	OUT0
IN1	OUT1
IN2	OUT2
IN3	
IN4	
IN5	
IN6	
IN7	

 


8-to-3 Encoder Schematic

 

8-to-3 Encoder Symbol

 

 8-to-3 Encoder Layout (Area $\approx 41 \times 87 \mu\text{m}$)



8-to-3 Encoder Extracted View

```

X11 Applications Edit Window Help
File Help

@(#)SCDS: LVS version 6.1.5 05/04/2012 23:29 (sjfdl224) $

Command line: /apps/cadence/ic6155/tools.lnx86/dfII/bin/32bit/LVS -dir /home/
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...

Net-list summary for /home/seas/bbernier/cadence/LVS/layout/netlist
count
30      nets
13      terminals
21      pmos
21      rmos

Net-list summary for /home/seas/bbernier/cadence/LVS/schematic/netlist
count
30      nets
13      terminals
21      pmos
21      rmos

Terminal correspondence points
N26      N7      IN0
N25      N10     IN1
N24      N5      IN2
N23      N4      IN3
N22      N2      IN4
N21      N6      IN5
N20      N12     IN6
N19      N9      IN7
N30      N3      OUT0
N29      N11     OUT1
N28      N8      OUT2
N18      N0      gnd!
N27      N1      vdd!

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nfet pfet rmos4 pmos4


The net-lists match.
```

8-to-3 Encoder LVS Report


Comparison Module

The comparison module compares the location of each of the three elevators in the elevator control unit.


Inputs	Outputs
ENC0	EL1En
ENC1	EL2En
ENC2	EL3En
EL1.0	
EL1.1	
EL1.2	
EL2.0	
EL2.1	
EL2.2	
EL3.0	
EL3.1	
EL3.2	

 


Comparison Module Schematic

 

Comparison Module Symbol

 

 Comparison Module Layout (Area $\approx 247 \times 631 \mu\text{m}$)



Comparison Module Extracted View

```

Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...

Net-list summary for /home/seas/bbernier/cadence/LVS/layout/netlist
count
719      nets
17       terminals
720      pmos
720      nmos

Net-list summary for /home/seas/bbernier/cadence/LVS/schematic/netlist
count
719      nets
17       terminals
720      pmos
720      nmos

Terminal correspondence points
N709      N10      EL1.0
N707      N26      EL1.1
N706      N37      EL1.2
N703      N38      EL1En
N718      N17      EL2.0
N717      N27      EL2.1
N716      N33      EL2.2
N715      N22      EL2En
N711      N30      EL3.0
N710      N8       EL3.1
N708      N35      EL3.2
N704      N23      EL3En
N714      N24      ENC0
N713      N4       ENC1
N712      N36      ENC2
N702      N1       gnd!
N705      N0       vdd!

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4

The net-lists match.

                                layout schematic
                                instances


```

Comparison Module LVS Report


Floor Calls Module

The floor calls module takes the elevator floor button presses and converts them into a 3 bit output. The module also checks to see if a button has been pressed.


Inputs	Outputs
CLK	ENC0
D0	ENC1
D1	ENC2
D2	EncOR
D3	
D4	
D5	
D6	
D7	

 

Floor Calls Module Schematic

 

Floor Calls Module Symbol

 

Floor Calls Module Extracted View (Area $\approx 143 \times 199 \mu\text{m}$)

```
@(#)$CDS: LVS version 6.1.5 05/04/2012 23:29 (sjfd1224) $
Command line: /apps/cadence/ic6155/tools.lnx86/dfII/bin/32bit/LVS -dir /home/seas
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...

Net-list summary for /home/seas/bbernier/cadence/LVS/layout/netlist
count
177      nets
15       terminals
166      pmos
166      rmos

Net-list summary for /home/seas/bbernier/cadence/LVS/schematic/netlist
count
177      nets
15       terminals
166      pmos
166      rmos

Terminal correspondence points
N163      N10      CLK
N176      N22      D0
N175      N18      D1
N174      N23      D2
N173      N17      D3
N172      N15      D4
N171      N16      D5
N170      N21      D6
N169      N24      D7
N168      N12      ENC0
N167      N11      ENC1
N166      N25      ENC2
N165      N5       Enc0R
N162      N1       gnd!
N164      N0       vdd!

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nfet pfet rmos4 pmos4

The net-lists match.


layout schematic
```

Floor Calls Module LVS Report


Elevator Module

The elevator module contains all the logic for the elevator to move up and down.


Inputs	Outputs
CLK	OUT0
IN0	OUT1
IN1	OUT2
IN2	
EncOR	
ENC0	
ENC1	
ENC2	
Compln	

 


Elevator Module Schematic

 

Elevator Module Symbol

 

 Elevator Module Layout (Area $\approx 178 \times 360 \mu\text{m}$)



Elevator Module Extracted View

```

X11 Applications Edit Window Help
File Help

@(#)SCDS: LVS version 6.1.5 05/04/2012 23:29 (sjfd1224) $

Command line: /apps/cadence/ic6155/tools.lnx86/dfII/bin/32bit/LVS -dir /home/se
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...

Net-list summary for /home/seas/bbernier/cadence/LVS/layout/netlist
count
345      nets
14       terminals
332      pmos
332      rmos

Net-list summary for /home/seas/bbernier/cadence/LVS/schematic/netlist
count
345      nets
14       terminals
332      pmos
332      rmos

Terminal correspondence points
N333      N48      CLK
N332      N50      CompIn
N341      N11      ENC0
N340      N23      ENC1
N339      N12      ENC2
N338      N10      EncOR
N336      N21      IN0
N335      N13      IN1
N334      N20      IN2
N344      N47      OUT0
N343      N22      OUT1
N342      N49      OUT2
N331      N1       gnd!
N337      N0       vdd!

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nfet pfet rmos4 pmos4

The net-lists match.

layout schematic
instances


```

Elevator Module LVS Report


Elevator Control Unit

The elevator control unit is the final design of the system.


Inputs	Outputs
CLK	OUT1.0
IN1.0	OUT1.1
IN1.1	OUT1.2
IN1.2	OUT2.0
IN2.0	OUT2.1
IN2.1	OUT2.2
IN2.2	OUT3.0
IN3.0	OUT3.1
IN3.1	OUT3.2
IN3.2	
Floor1	
Floor2	
Floor3	
Floor4	
Floor5	
Floor6	
Floor7	

 


Elevator Control Unit Schematic

 

Elevator Control Unit Symbol

 

 Elevator Control Unit Layout (Area $\approx 780 \times 760 \mu\text{m}$)



Elevator Control Unit Extracted View

```

X11 Applications Edit Window Help
File Help

IN2.2      N1865      N30
IN3.0      N1889      N21
IN3.1      N1888      N2
IN3.2      N1885      N33
OUT1.0     N1872      N15
OUT1.1     N1870      N34
OUT1.2     N1869      N29
OUT2.0     N1892      N22
OUT2.1     N1891      N16
OUT2.2     N1890      N23
OUT3.0     N1874      N6
OUT3.1     N1873      N9
OUT3.2     N1871      N10
gnd!       N1868      N1
vdd!       N1876      N0

ut not in the rules:
not in the netlist:
os4 pmos4

layout schematic
instances
0 0
0 0
0 0
0 0
3764 3764
3764 3764

nets
0 0
0 0
0 0
1893 1893
1893 1893

terminals
0 0
0 0
28 28

eas/bbernier/cadence/LVS/schematic

Devices in the netlist b
pcapacitor
Devices in the rules but
cap nfet pfet nua
The net-lists match.

un-matched
rewired
size errors
pruned
active
total

un-matched
merged
pruned
active
total


un-matched
matched but
different type
total

Probe files from /home/s


```

Elevator Control Unit LVS Report


Elevator Control Unit Pad

 

Elevator Control Unit Pad Symbol

 

Elevator Control Unit Pad Layout

 

Elevator Control Unit Extracted View

4. Testing Procedures


If this chip were to be fabricated, the testing procedure would be very similar to the simulations performed within Virtuoso. Inputs would need to be set up in a similar fashion and timed to recreate the simulation. There would need to be buttons capable of outputting pulses that last for at least 2 clock cycles to ensure the control unit receives the input. The outputs could be hooked up to a microcontroller capable of reading the values and converting them to decimal digits to display what floor the elevator should be on. It could also do this at a delay, because the control unit itself will change the floor every clock cycle, which would be indistinguishable to the human eye.

Obviously, the chip could not be tested exhaustively because the number of states and possible inputs is immense. It would need to be assumed that any test situation thrown at it would be representative of real world use cases and a variety of them could be tested, just not all.

 5. Overall System Results

Critical System Specifications

- Total Transistor Count: 3764
- Total Area: $780 \times 760 \mu\text{m} = 0.5928 \text{mm}^2$
- Maximum Operating Frequency: $\sim 40 \text{MHz}$
- Minimum Input Pulse: $2 \times \text{Clock Period}$
- Average Power Consumption:
 - Without PAD Frame: $7.088 \mu\text{W}$
 - With PAD frame: $139.3 \mu\text{W}$
- D Flip Flop Setup/Hold Time:
 - Setup Time: 62ps
 - Hold Time: 953ps




Test to Find Setup and Hold Time


Two parametric simulations were run to find the set and hold time for the D Flip Flop. First, the start of the input pulse was varied to determine how long before the clock pulse it needed to go high to have the output follow as expected. Once the set time was determined, the length of the input pulse was varied to see how short it could be made and still get the correct output. This allowed us to compute both the set and hold times determined above.

Also important to note, the maximum operating frequency was found to be roughly 40MHz before the operation of the system began to seriously degrade. This, however, is not extremely important in the design because it simply needs to be clocked fast enough to get the input pulses from the elevator buttons. A single button press is usually longer than 10ms, so a much slower frequency would suffice. The elevators also are not moving between floors that fast, so this does not affect clock time either. All simulations were run off a 40KHz clock.

Final System Simulations

 


Simulation Results off Schematic View

 


Overall Test 1 from PAD Frame

Overall Test 1 shows multiple calls for an elevator at the first floor. Each elevator starts uninitialized in the 0 state, and must then initialize its register to 1 at each call for an elevator. When all the elevators are on the same floor, it is built into the chip that Elevator 1 would take the task. Similarly, if 2 and 3 were at the same floor and closest to the call for an elevator, Elevator 2 would go instead of Elevator 3. Here, Elevator 1 responds to the first call, coming to floor 1 and holding until it receives an input from within the car to move to floor 6. It then proceeds to output 2, 3, 4, 5, and finally 6 steadily once it reaches that point. On the next call, Elevator 2 responds and is told to go to floor 4. Finally, Elevator 3 gets called to go to floor 5. At the very end, a final call at floor 1 requires the system to decide which elevator is closest, with them now being at floors 6, 4, and 5, respectively. It correctly chooses to send Elevator 2 because it is closest and that elevator begins moving down to floor 3 as can be seen at the far right of the test.

 


Overall Test 2 from PAD Frame

This test is similar to the previous one in that it has multiple calls, however, this time from multiple floors. The elevators respond accordingly, and it is important to note that Elevator 2 responds to both the 2nd and 3rd calls at the 1st and 5th floors, respectively. It completes a request to go to the 4th floor, then gets a call from the 5th floor because it is only 1 floor down. Elevator 3 responds to the final floor 1 call, however, floor 1 is pressed inside the elevator, so it remains there and waits on another input.

 

 Extracted Simulation without the PAD Frame Showing Power Consumption



Extracted Simulation with PAD Frame Showing Power Consumption

In the simulations with power consumption, it was interesting that the average power found with the PAD frame was much higher than that simulated without it. This is most likely simply due to the case that the simulations performed without the PAD frame did not take into account the input capacitances as well as those on the outputs. The PAD frame simulation is obviously more realistic to what may be found in real life. Another interesting note is that without the PAD frame, the power peaks were actually close to momentary spikes at 3W, but with the PAD frame, the spikes were only 1W.

6. Conclusion

In conclusion, this project provided students with the opportunity for hands on design and layout of an ASIC. Students used the knowledge they built throughout the class lectures and lab sessions to complete a functional design and layout the entire design for fabrication. The project used industry standard tools necessary to success in the VLSI field. The specific elevator control unit project posed many challenges that were not initially taken into consideration. For one, the actual design of the schematic to fulfill the necessary logical requirements was much harder than anticipated. The control unit is dependent upon a lot of control logic, not simply chaining a lot of gates together to perform an operation. Each component had to be carefully thought out to produce the desired decision. When it came to the layout, this also proved challenging because it was a connection of many random gates as opposed to a uniform setup of many of the same blocks. Overall, the challenges were mainly overcome and the project was a success. In the future, it would be useful to add more realistic functionality to the elevator such as up and down buttons at each floor; however, under the time and area constraints for this project, the chip is pretty versatile.

7. References

[1] Chandrakasan, Anantha, Borivoje Nikolic, and Jan M. Rabaey. *Digital Integrated Circuits: A Design Perspective*, 2nd ed. Prentice Hall, 2003.